

# EE518 - POWER CONVERTER ANALYSIS AND DESIGN LAB

Presented by –Shubham Raj (2023EEM1052)  
Shubham Faujdar (2023EEM1051)

# HARDWARE IMPLEMENTATION OF BUCK-BOOST CONVERTER

## Component used:

1-phase transformer 230v | | 15-0-15v

Mosfet(irf460), TLP-250, Voltage Regulator(IC 7815)

Diode(1N4007), LED , Diode Bridge Rectifier(DBR)

Resistance (33 ohm) , (1 k ohm)



Inductance 1.6 milli Henry ..... (1)

Filter capacitance 47 micro farad(100v)(1)


## Rating of BUCK-BOOST:

- Variable Dc input volatges : 1 to 30 (volt).
- Power Rating : 50 watts.
- Inductor value: 1.6 milli henry.
- output capaciotor : 47 micro farad.
- output Resistance : 33 ohm.
- Variable Duty cycle:0-1.


## Hardware :

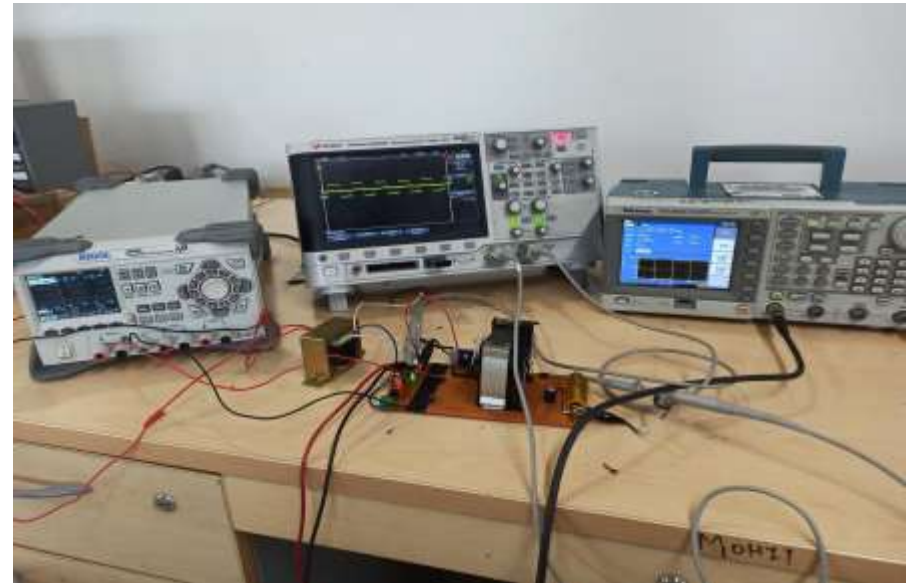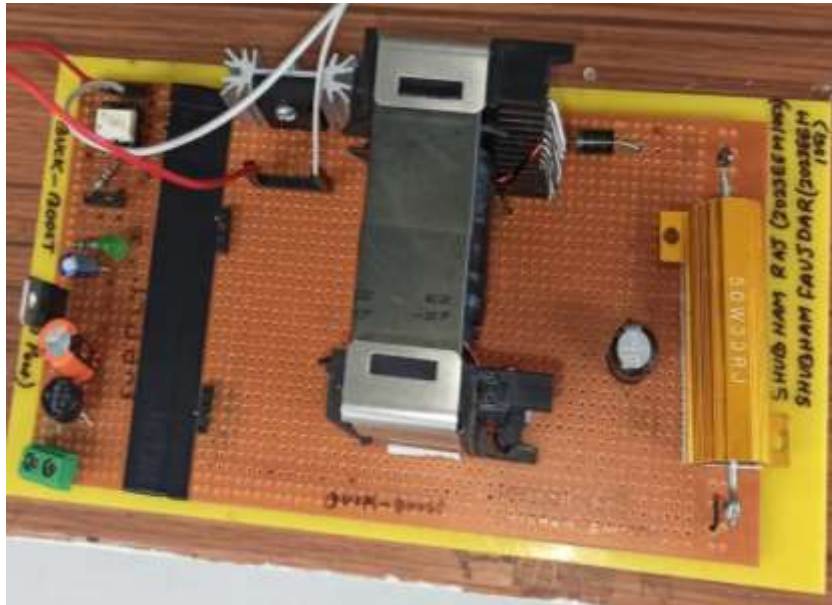



## SIMULATION RESULTS:

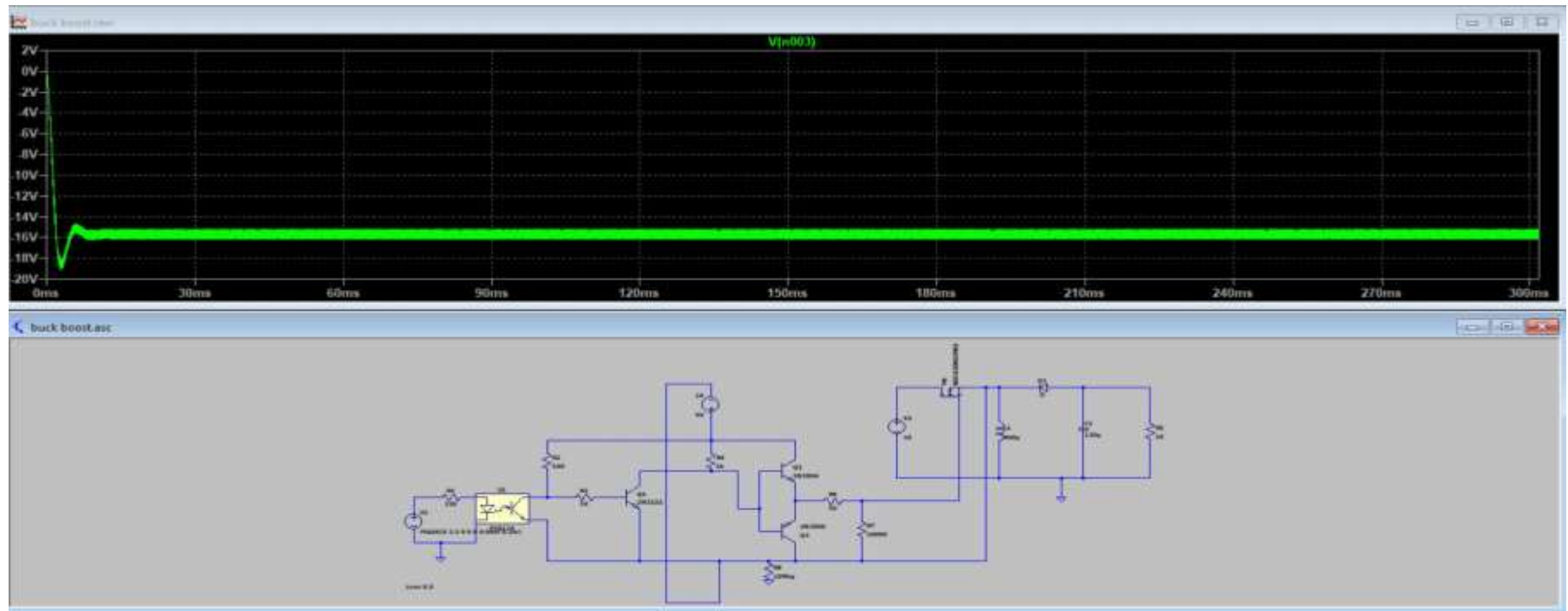


## HARDWARE RESULTS:(BUCK-MODE)

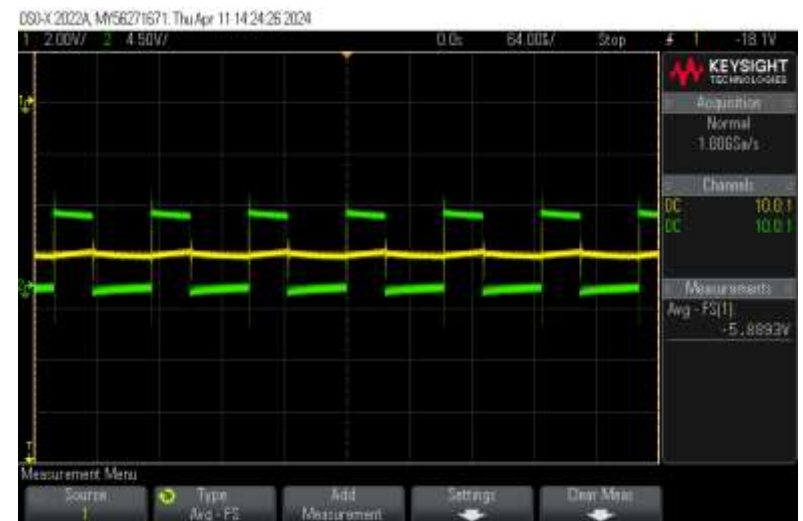

## HARDWARE RESULTS : (BOOST MODE)

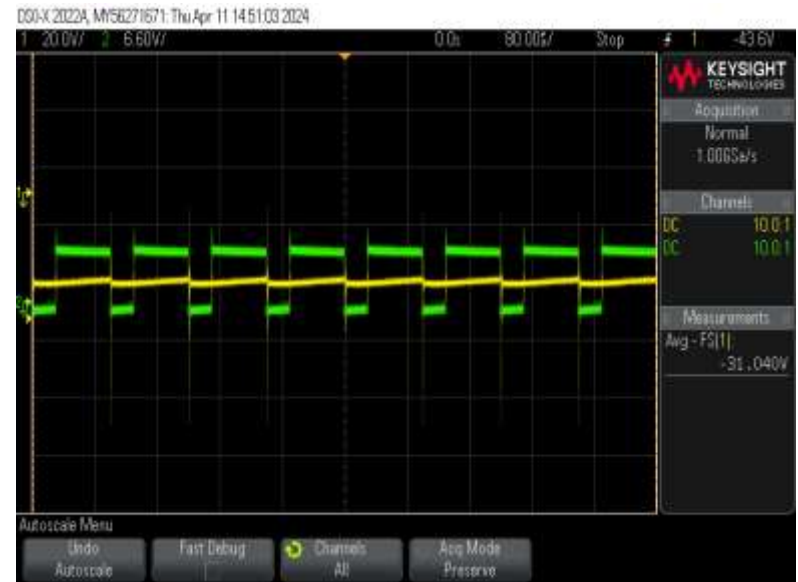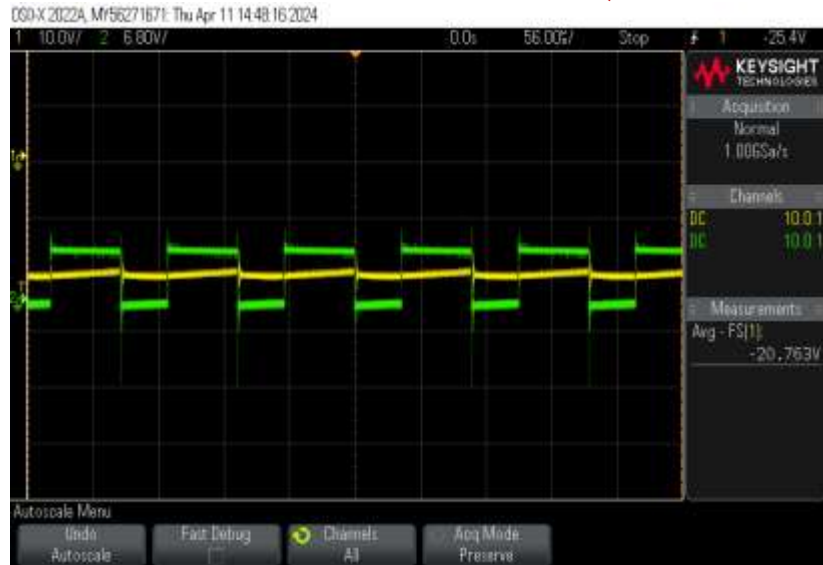

Duty=0.5 Vin=10v and Vout=9.123v

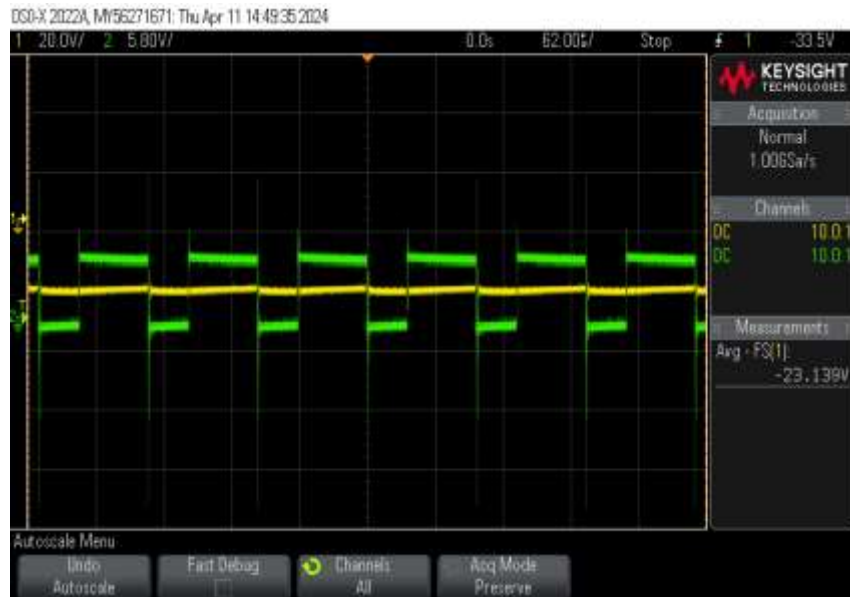

THANK YOU